

A Power-Distribution Switch With Latched Overcurrent Protection

Edward Jung

PMP - Systems Power

ABSTRACT

Power-distribution switches, like the TPS203x, operate in retry mode in an overload, but some applications require the switch to latch off. The latch-off function can be implemented using the simple circuit described in this application report.

1 Introduction

The Texas Instruments TPS202x, TPS203x, TPS204x, TPS205x, TPS206x, TPS208x, and TPS209x power distribution switches limit the current into a fault by switching to constant-current mode. If a fault causes the switch junction-temperature to rise above a preset level, then a thermal protection circuit shuts off the switch to prevent damage. Recovery from thermal shutdown is automatic once the switch has cooled sufficiently. In a sustained fault, the switch cycles between current limit and thermal shutdown. In some systems, it may be preferable to simply latch off the switch under this condition. In a battery-powered system like a laptop computer, for example, latching off the switch has the advantage of eliminating unnecessary battery drain by a *dead* load. This latch-off function can be implemented with a few inexpensive and readily available logic gates around the switch.

2 Latching Off Is Easy

The circuit in [Figure 1](#) uses a SN74HC00 quad-NAND gate to implement overcurrent latch off. The SN74HC00 high-speed CMOS logic gate is selected for this application, not for its speed, but because it operates over the 2.7-V to 5.5-V range of the TPS2034D switch.

The TPS2034D switch is active-high enable. An active-low enable switch like the TPS2014 must be driven by the U1:A output instead of U1:B output.

At power up, ENABLE must be at logic 0 until VCC is stable to ensure that the switch initializes in the off state. After VCC is stable, logic 1 at ENABLE turns on the switch. In an overcurrent condition, OC# momentarily pulls low which latches FAULT# at logic 0 and disables the switch. The host can monitor FAULT# for an overcurrent condition. Toggling ENABLE resets FAULT# and re-enables the switch.

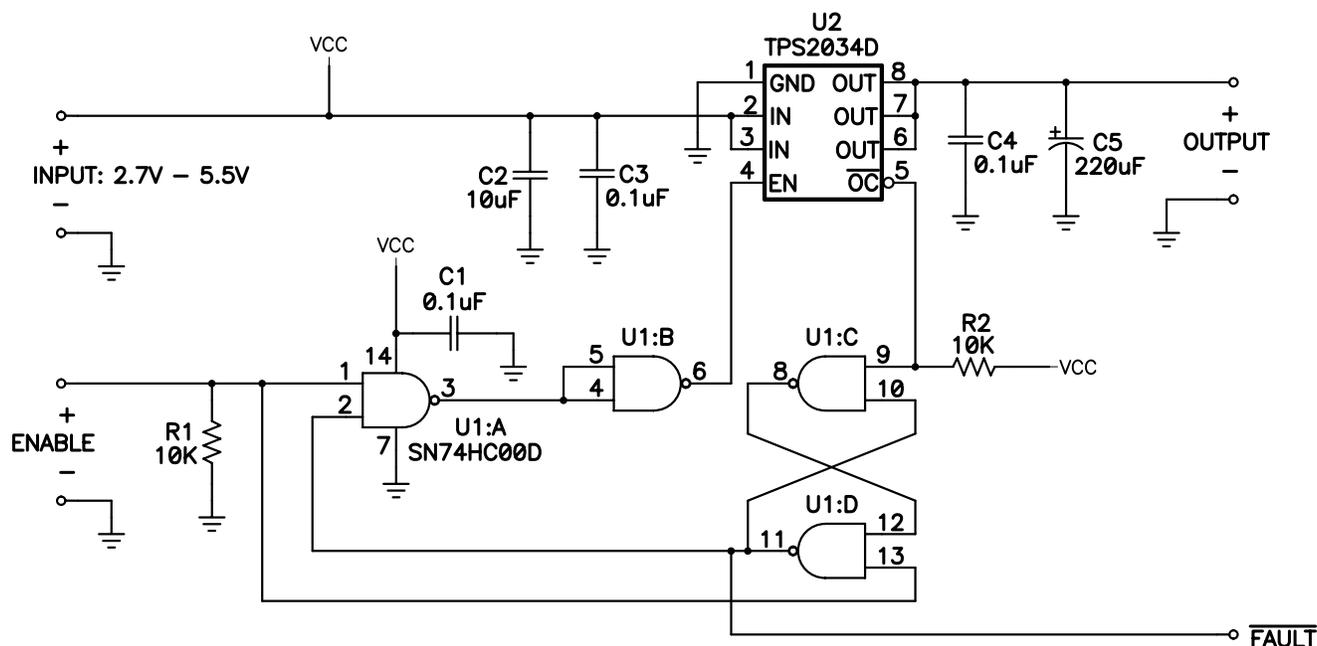


Figure 1. Overcurrent Latch Off Using Quad-NAND Gate

3 Circuit Performance

For the waveforms in [Figure 2](#) through [Figure 4](#), CH1 = ENABLE, CH2 = OC#, CH3 = FAULT#, and CH4 = Current at the 2.7-V to 5.5-V input.

[Figure 2](#) shows the circuit waveforms if the switch is enabled into a 2-Ω load.

[Figure 3](#) shows the circuit waveforms if the switch is enabled into a dead short.

[Figure 4](#) shows the circuit waveforms if the enabled-switch output is short circuited. The input-power distribution resistance specific to this set-up and the high surge current cause the channel 1 and channel 2 voltages to droop when the switch output is short circuited.

Note that OC# (channel 2) pulls to logic 0 for a brief period in an overcurrent condition. The OC# output is not as useful a fault indicator as is the FAULT# output.

The load inrush-current must be less than the short-circuit output current (I_{OS}) of the switch to prevent the switch from turning off prematurely when enabled. This can limit the amount of load bypass-capacitance.

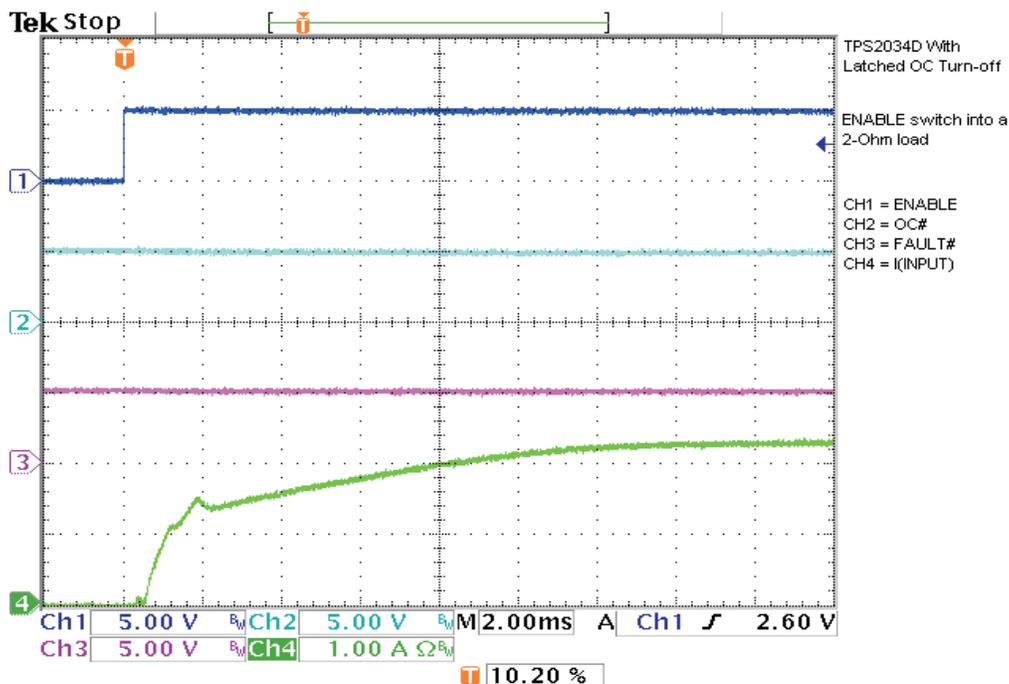


Figure 2. Switch Is Enabled Into 2- Ω Load

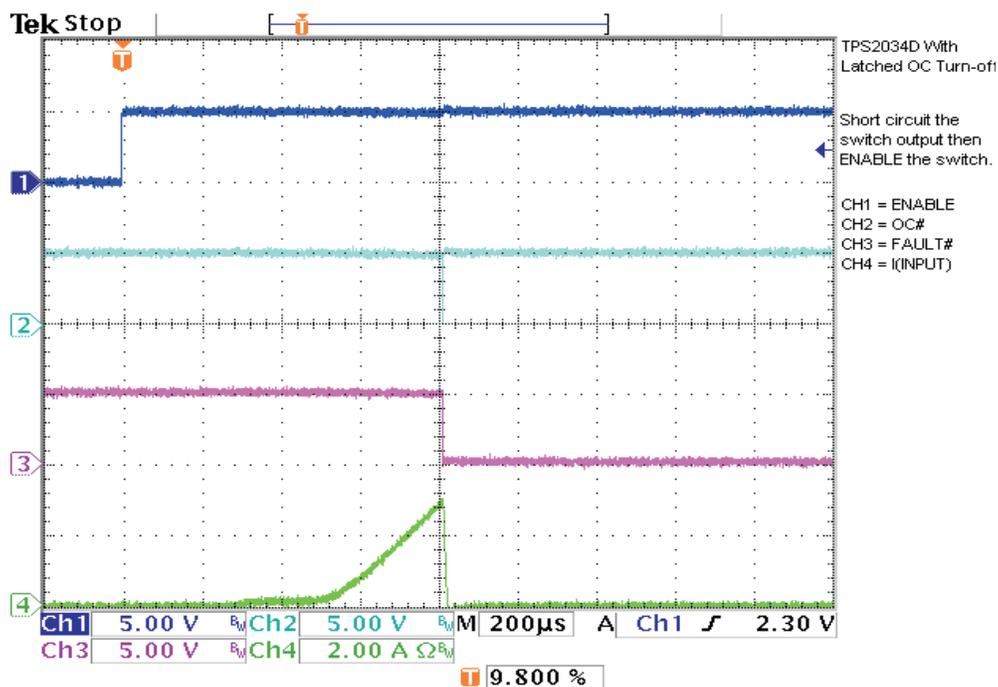


Figure 3. Switch Is Enabled Into Short Circuit

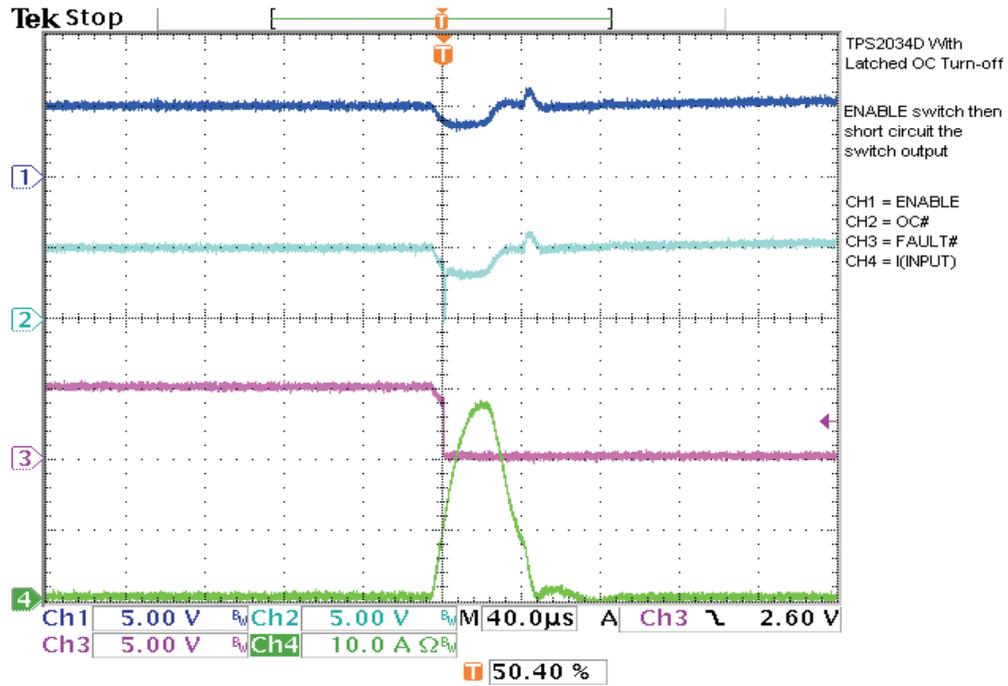


Figure 4. Enabled-Switch Output Is Short Circuited

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| Products | | Applications | |
|-----------------------|--|---------------------|--|
| Amplifiers | amplifier.ti.com | Audio | www.ti.com/audio |
| Data Converters | dataconverter.ti.com | Automotive | www.ti.com/automotive |
| DSP | dsp.ti.com | Broadband | www.ti.com/broadband |
| Interface | interface.ti.com | Digital Control | www.ti.com/digitalcontrol |
| Logic | logic.ti.com | Military | www.ti.com/military |
| Power Mgmt | power.ti.com | Optical Networking | www.ti.com/opticalnetwork |
| Microcontrollers | microcontroller.ti.com | Security | www.ti.com/security |
| RFID | www.ti-rfid.com | Telephony | www.ti.com/telephony |
| Low Power Wireless | www.ti.com/lpw | Video & Imaging | www.ti.com/video |
| | | Wireless | www.ti.com/wireless |

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated