

Differences Between UCC3817A/18A/19A and UCC3817/18/19

Mike O'Loughlin

System Power

ABSTRACT

The UCC3817A/18A/19A family of PFC controllers (UCC3817A family) is pin for pin compatible with the UCC3817/18/19 family of devices (UCC3817 family). The output stage of UCC3817A family has been updated to allow use of a smaller external gate drive resistor values. For some power supply designs where an adequately high enough gate drive resistor can not be used, the UCC3817A family offers a more robust output stage at the cost of increasing the internal gate resistances. The gate drive of the UCC3817A family however remains strong at 1.2 A of peak current capability (I_{MAX}).

This paper highlights the differences in the gate drives of the two device families.

Gate Drive Changes

- The high side (sourcing) DMOS output structure used in the original UCC3817 family is replaced with a high voltage PMOS structure. A small series resistor RLS (2 Ω) has also been added to low side DMOS structure.
- The pull up resistance (R_{pullup}) on the gate drive (DRVOUT) was increased from 5 Ω to 9 Ω .
- The pull down resistance ($R_{pulldown}$) on DRVOUT was increased from 2 Ω to 4 Ω .

Effects in the Application

In a typical application it is required to use a current limiting/damping resistance for the gate drive of the MOSFET.

- This resistor needs to be sized based on the pull down resistance ($R_{pulldown}$) and the maximum gate drive current (I_{MAX}); as well as, the maximum VCC voltage (VCC).

$$R_{GATE} = \frac{VCC - (I_{MAX} \times R_{pulldown})}{I_{MAX}} \quad (1)$$

- In the case of the UCC3817A with a maximum VCC voltage of 18 V this would require a resistance of roughly 11 Ω .
- This 11- Ω resistor would limit the source current to roughly 900 mA and the sink current to roughly 1.2 A.
- In comparison, R_{GATE} for the UCC3817 device in this application would be roughly 18 Ω .

Summary

The changes in gate drive circuitry have little effect in a typical application except allowing the designer to decrease the size of the gate drive resistor. The equation above for selecting a gate drive resistor is only for the UCC3817A family of devices. When selecting the gate drive resistor for the standard UCC3817 family please use the resistor selection graph that is published in the UCC3817/UCC3818 data sheet.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2003, Texas Instruments Incorporated