


## Uninterruptible Synchronization Clock Circuit

*SVA - SimpleSwitcher*

Devices that utilize a phase-locked loop (PLL) for accepting an external clock signal for synchronization, may not operate as expected if the external clock is removed. Once the PLL recognizes a clock is present, the device relies on the PLL to control the switching frequency and ignores the frequency setting resistor. However, if the PLL is controlling the switching frequency and the external clock is removed, the PLL waits for a clock pulse that never comes. There is a time-out period that the PLL must wait before it recognizes that no clock is present and switches to the frequency setting resistor. During the time-out period, the PLL frequency decreases. The time-out period could be long enough to cause problems for your system, such as over-current or increased ripple. For the LMZ3 Simple Switcher power modules the switching frequency drops to approximately 100 kHz before returning to the switching frequency set by the RT resistor.

Using a CMOS 555 timer (such as LMC555) configured as shown in [Figure 1](#), between the external synchronization clock signal and the RT/CLK pin of the LMZ3 power module, will ensure a clock signal is present at the RT/CLK pin even if the external clock signal goes away. In this configuration, as long as the external synchronization clock is present, the clock pulses at the output of the 555 timer will be at the same frequency as the clock signal at the RESET pin. However, if the external synchronization clock is disabled, the 555 timer will continue to output clock pulses at the frequency set by the external R and C, without missing a pulse. **The external clock signal must be programmed to a High state when the clock is disabled (if not, the signal can be inverted before the 555 timer).** The frequency of the 555 timer should be programmed to approximately the same frequency as the external clock for the most seamless transition when the external clock is removed.

[Figure 1](#) shows the schematic of an external synchronization clock feeding the RESET pin of a 555 timer and the output of the 555 timer is feeding the RT/CLK pin of an LMZ3 device. The values for R and C can be selected from [Table 1](#) or can be calculated using [Equation 1](#). The scope shot in [Figure 2](#) shows the external sync clock on trace 2 (blue). The clock pulses are present at first, then the clock goes away (High), and then the clock starts switching again. Trace 1 (pink) shows the clock pulses at the OUT pin of the 555 timer, feeding the RT/CLK pin of the LMZ3 device. Notice that the clock pulses feeding the RT/CLK pin of the LMZ3 device never go away. During the period when the external clock pulses are missing, the 555 timer produces the clock.

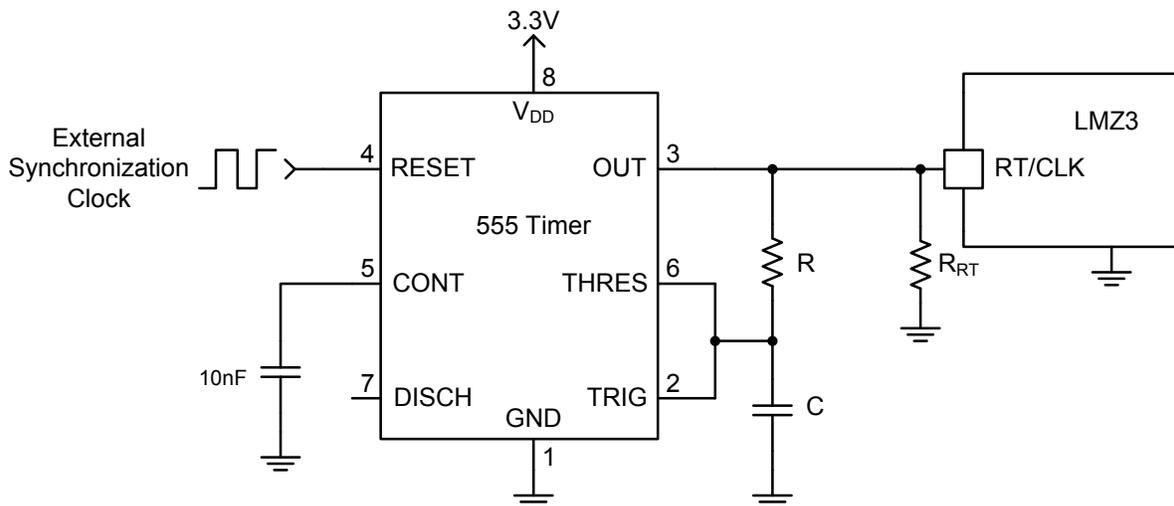


**Figure 1. 555 Timer Uninterruptible Clock Circuit**

$$\text{Freq} = \frac{1}{1.4 \times (R \times C)} \tag{1}$$

**Table 1. 555 Timer Frequency Setting**

Freq (kHz)	250	300	350	400	450	500	550	600	650	700	750
R (kΩ)	13	11	9.31	8.25	7.32	6.49	5.9	5.49	4.99	4.64	4.32
C (pF)	220	220	220	220	220	220	220	220	220	220	220

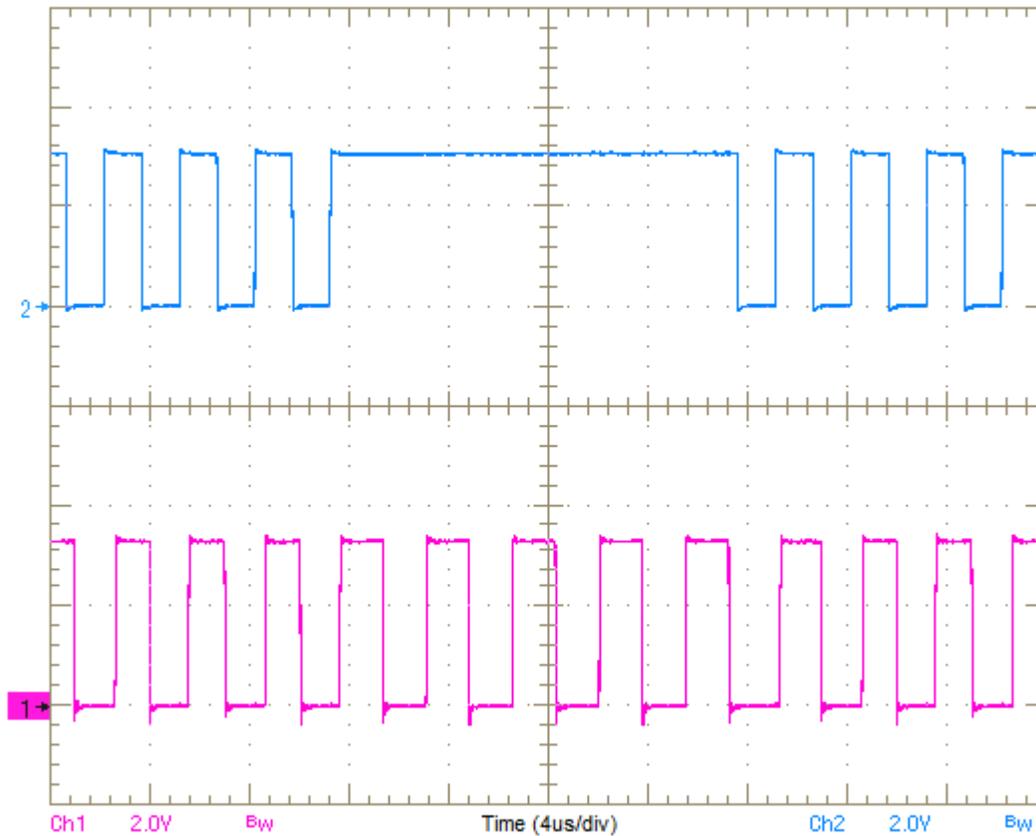

**Figure 2. Sync Clock and 555 Timer Output Pulses**

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)